


# Power Controller

Josh Wilkins -- 9/19/2019


# Imports↔

#CSS↔

## ADL6010 with HMC694 VGAs

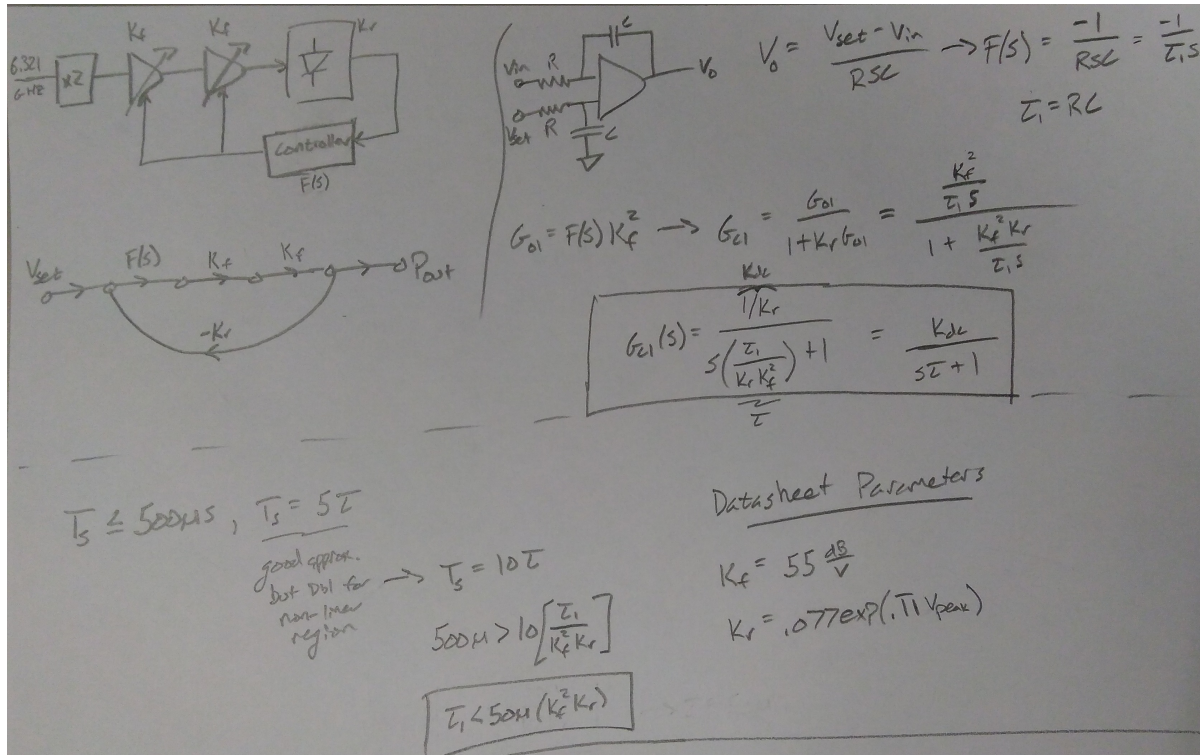


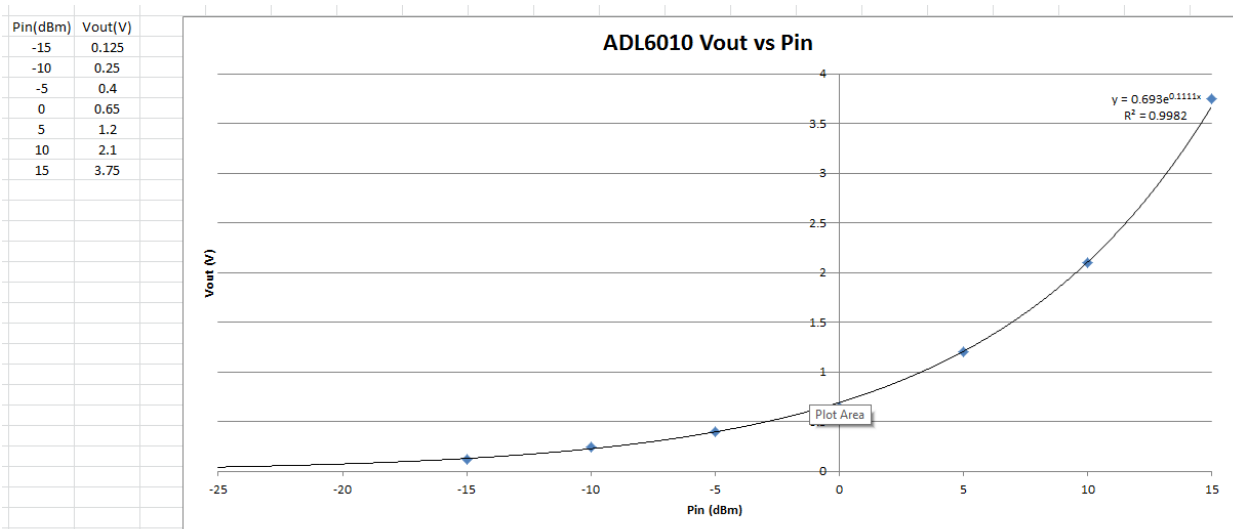From the ADL6010 Datasheet,  $K_r$  is given as a linear value in V/V. But in the V/dBm units needed, it is very nonlinear as shown below. Taking the derivative of the graph below, the value of  $k_r$  in units of V/dBm can be approximated.




► # Designing the Controller using the slowest response for  $K_r$  so that the settling

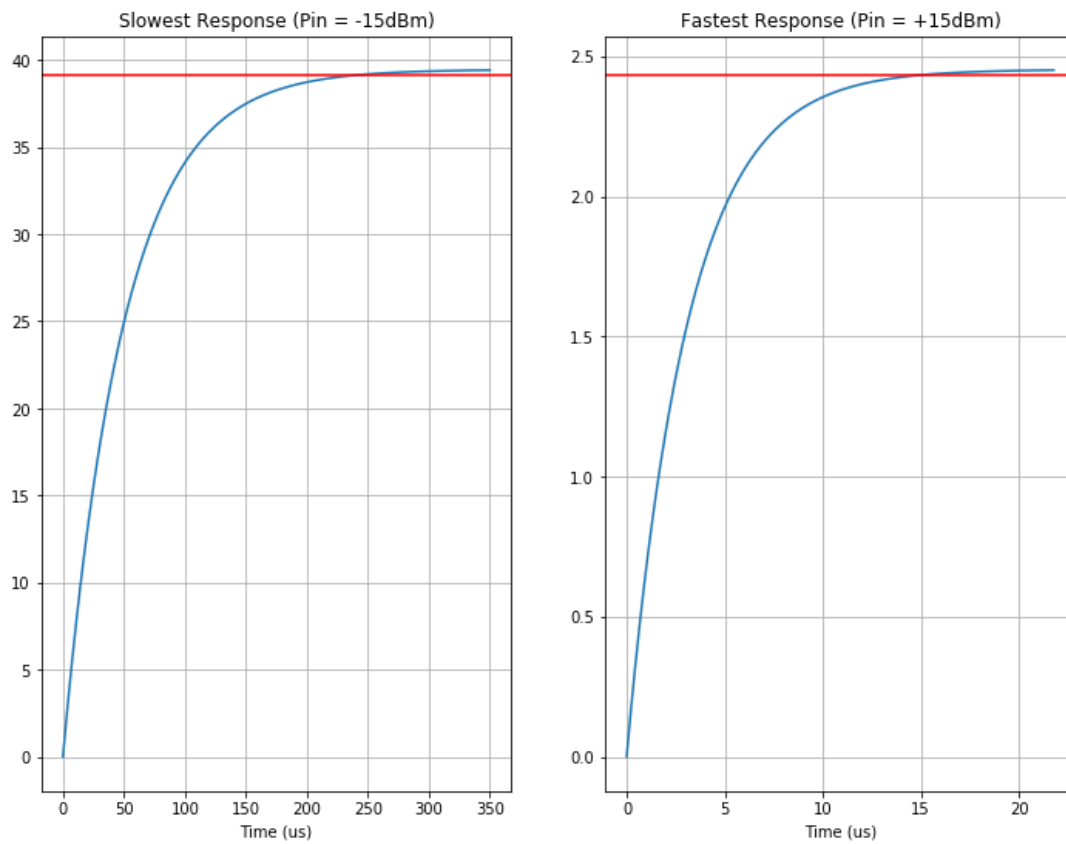$R=3833.9 \text{ Ohms}$        $C=1.0\text{e-}06 \text{ uF}$




► # Bode Plots↔

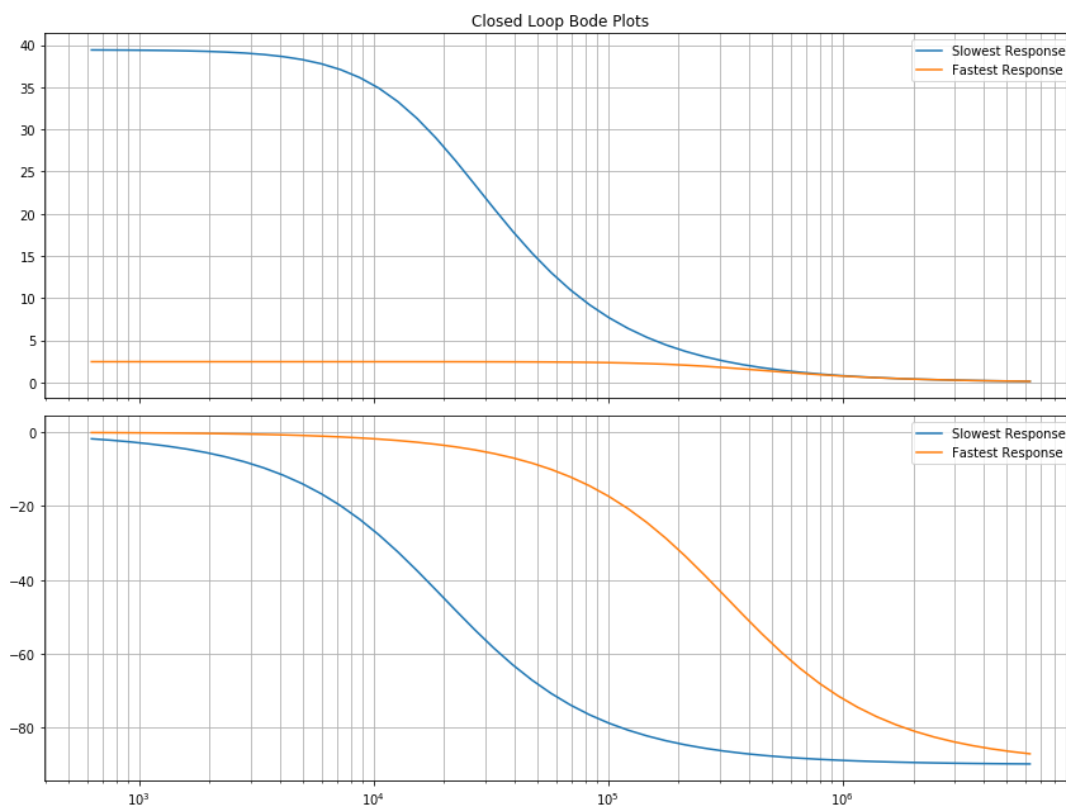


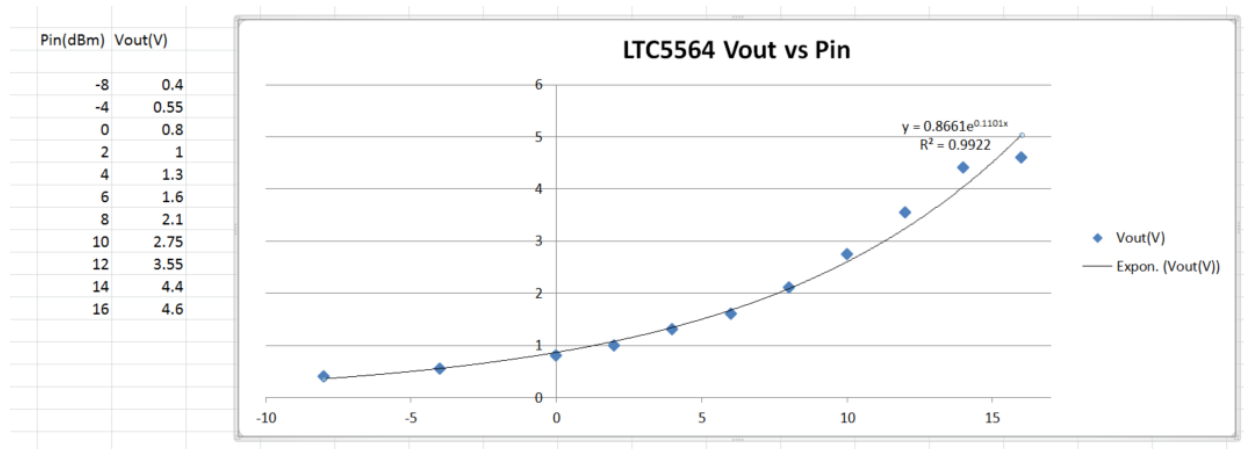
## LTC5564 with HMC694 VGAs

Due to the long lead time of the ADL6010, the LTC5564 was also examined for use. It appears to have a similar response, however it looks like it will be unusable due to its temperature dependency. Again, using the data from the datasheet to estimate  $\tau$ :




► # Designing the Controller using the slowest response for  $\tau$  so that the settling

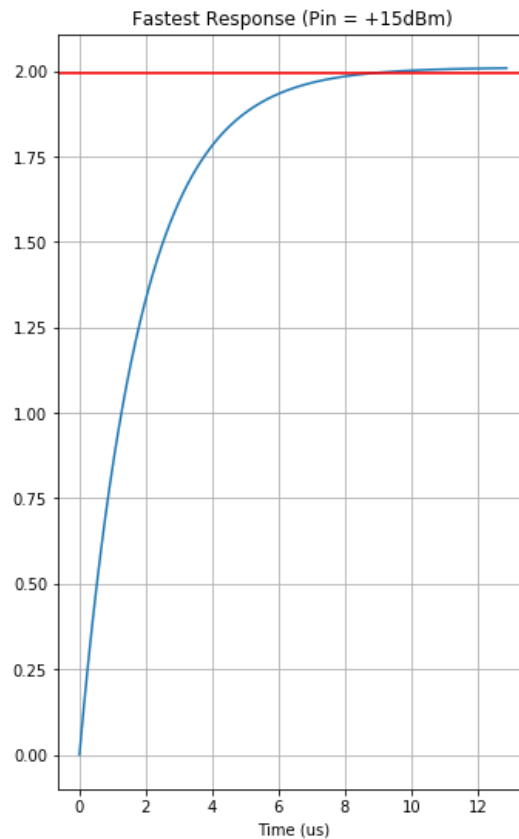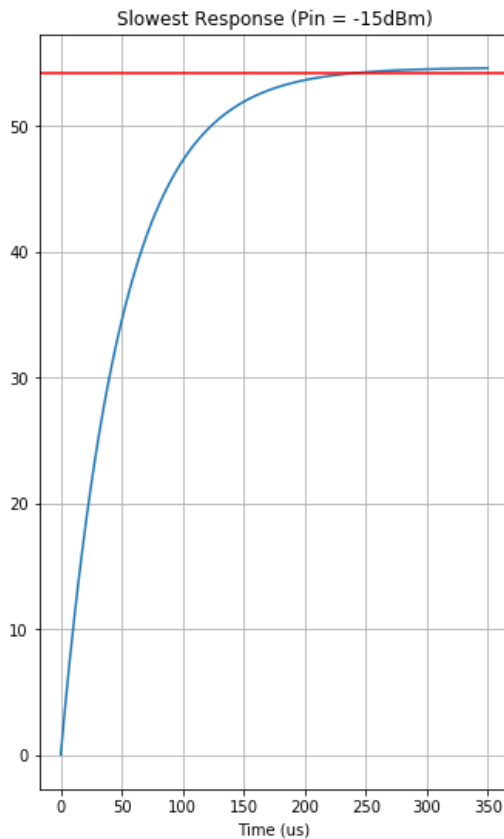
$R=1844.7 \text{ Ohms}$        $C=1.5e-06 \text{ uF}$



## # Bode Plots↔

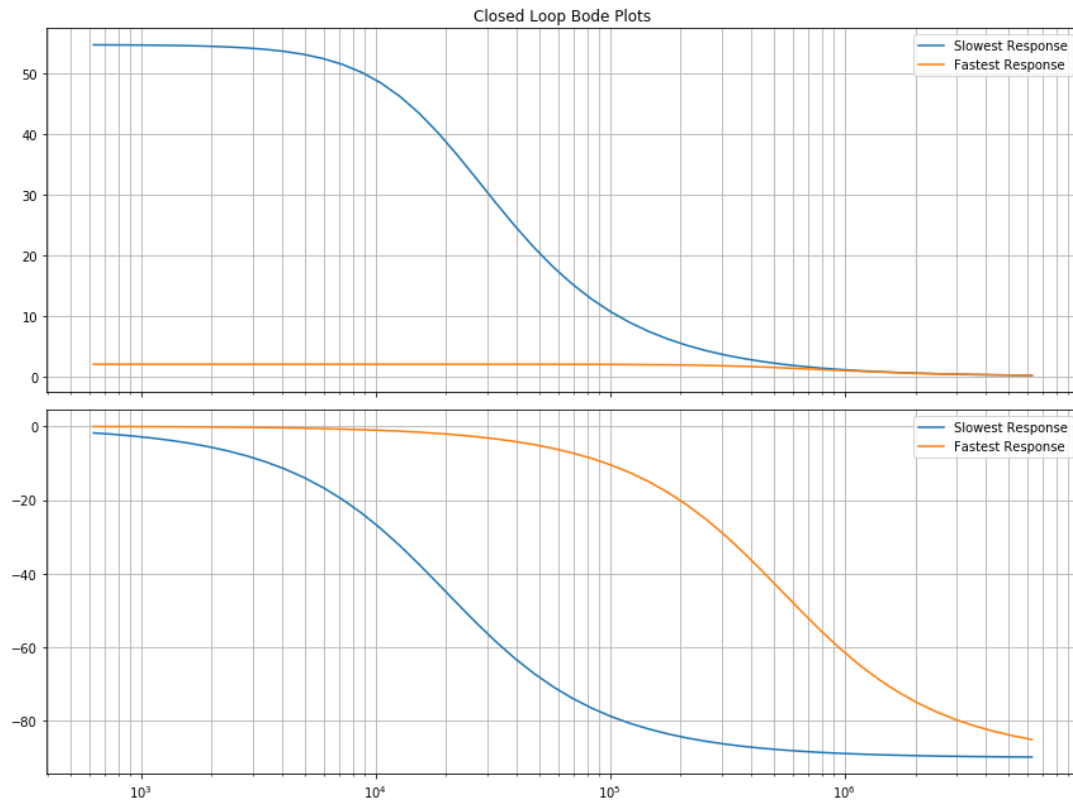


## ADL6010 with HMC712 VVA

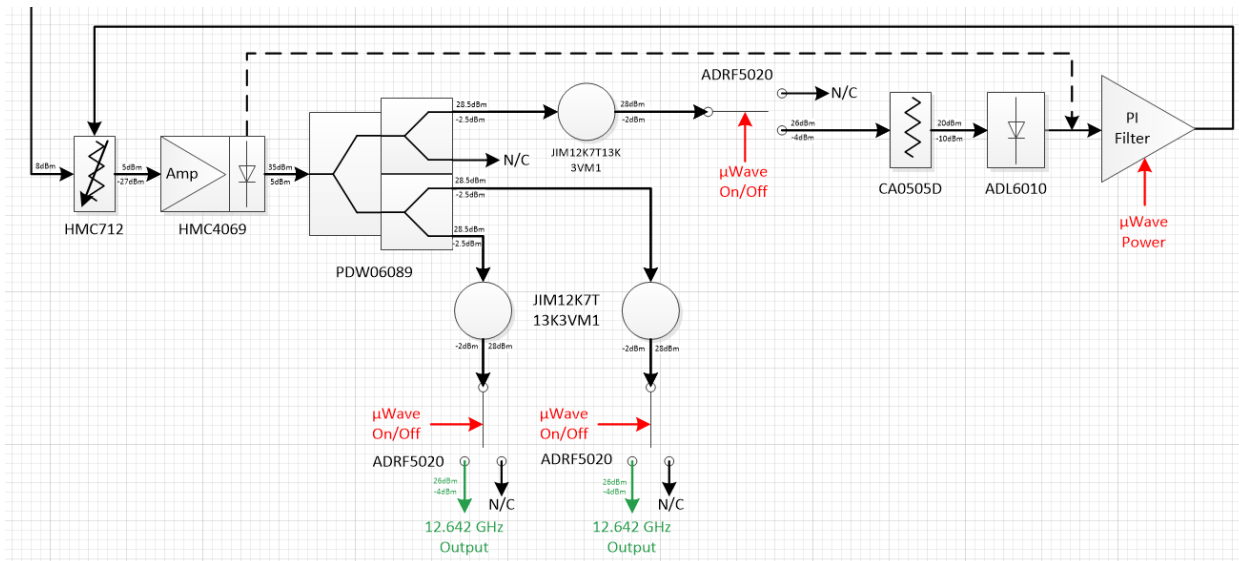

► # Designing the Controller using the slowest response for Kr so that the settling

R=3976.6 Ohms      C=1.8e-09 uF

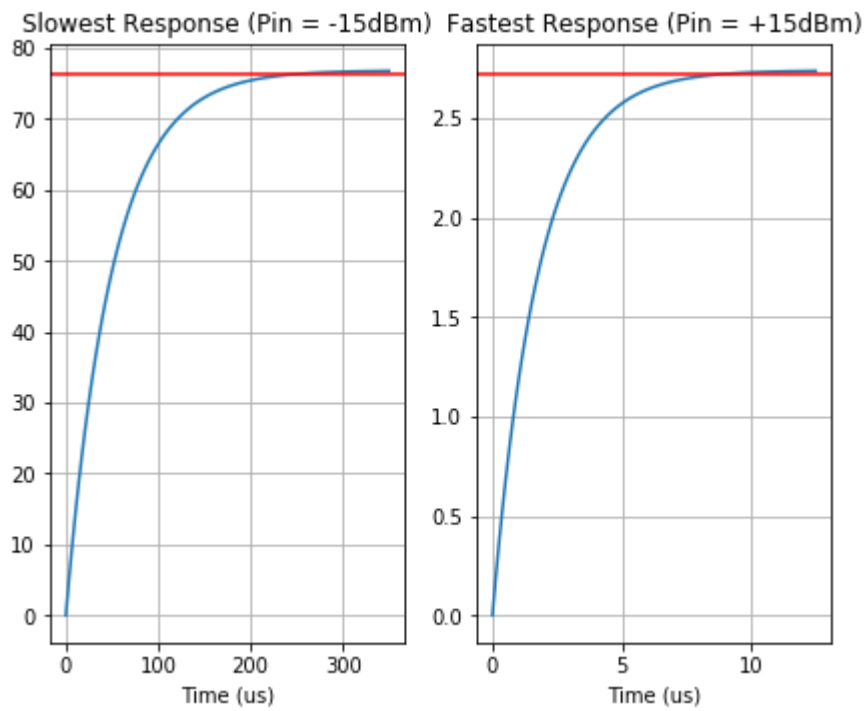

► # Bode Plots↔

